

CSE 3203 CT 4 Assignment
Roll No: 1803163

Assignment Problem:

Build CPU based on following requirements:

1. Word Size of CPU = 4
2. ALU Operations = XOR, ADD, ROR
3. Register Number = 4
4. Size of RAM = 7
5. Word size of ISA and RAM = 15
6. CPU Instructions = Register Mode, Immediate Mode, JMP, JG

Solution:

Simulator Design:

1. [ALU Circuit \(Top to Bottom all circuits\):](#)

 


Figure: 4bit XOR

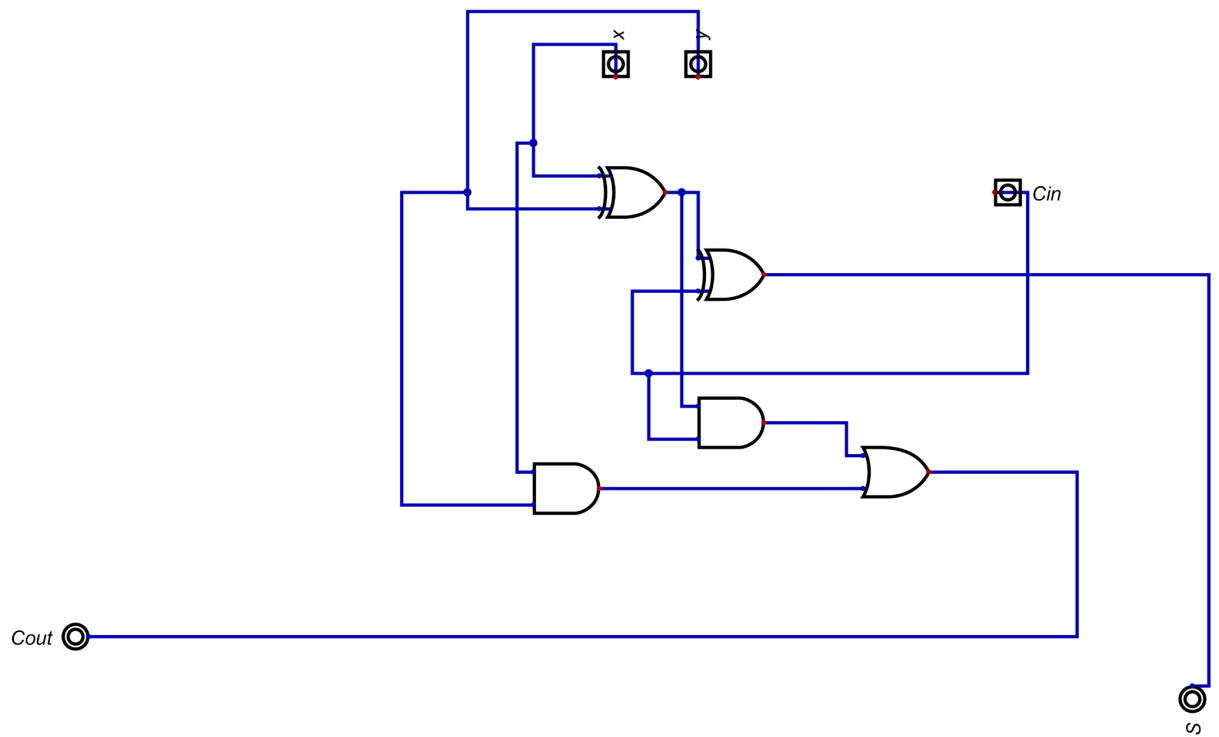


Figure: Full Adder

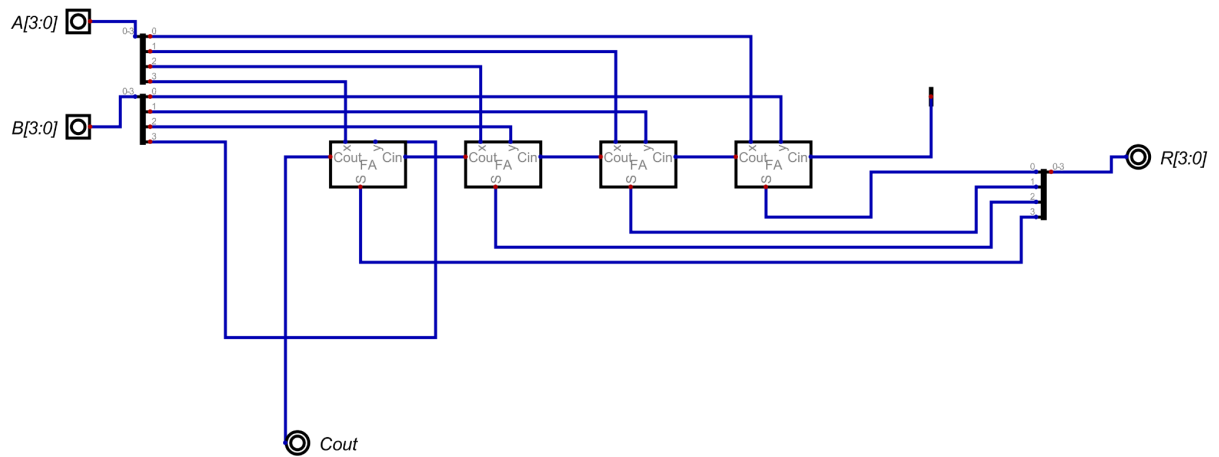


Figure: 4bit Adder

 


Figure: 4bit ROR

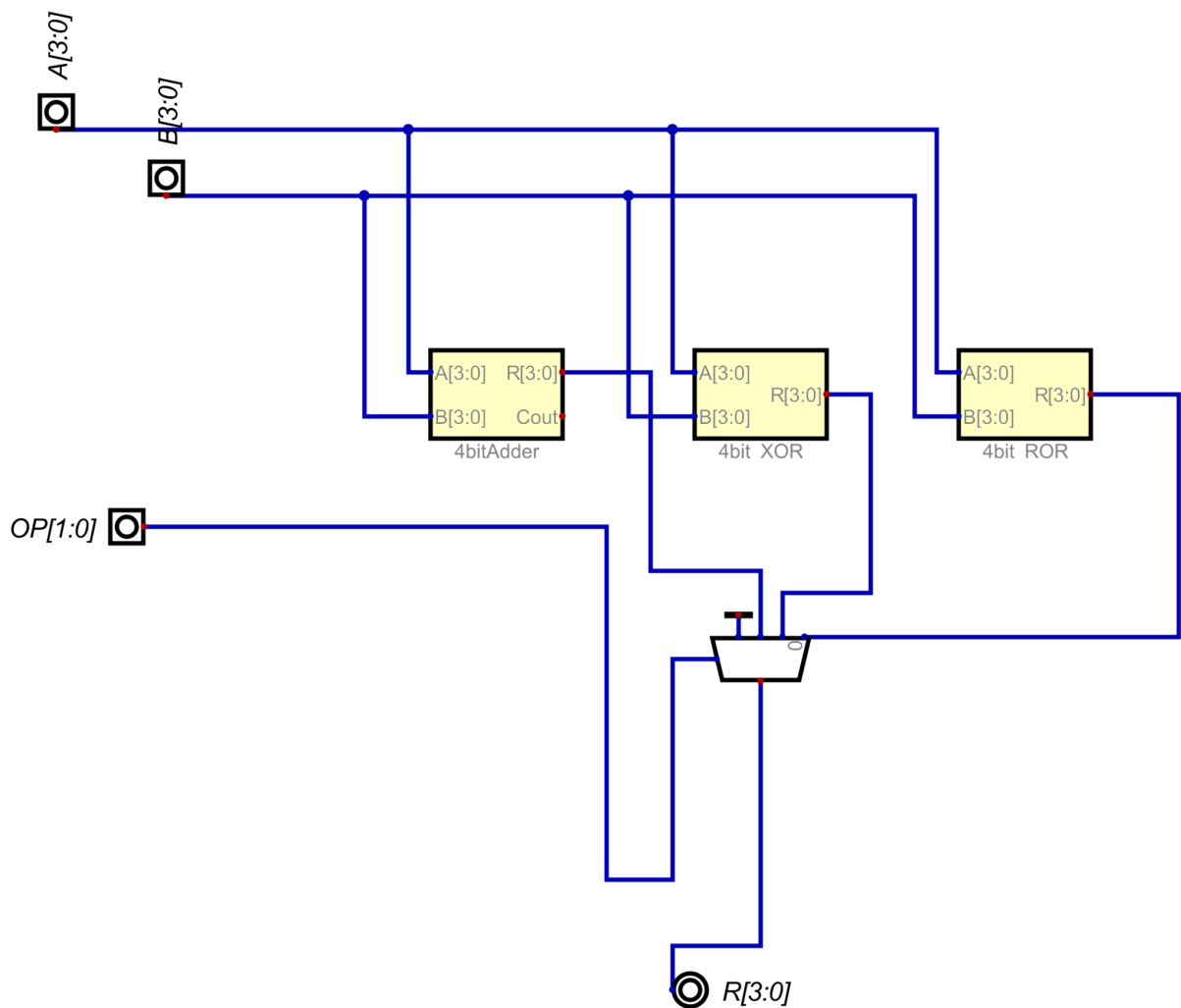


Figure: 4bit ALU

2. Register Set Circuit (Top to Bottom all circuits):

 


Figure: 1bit Register

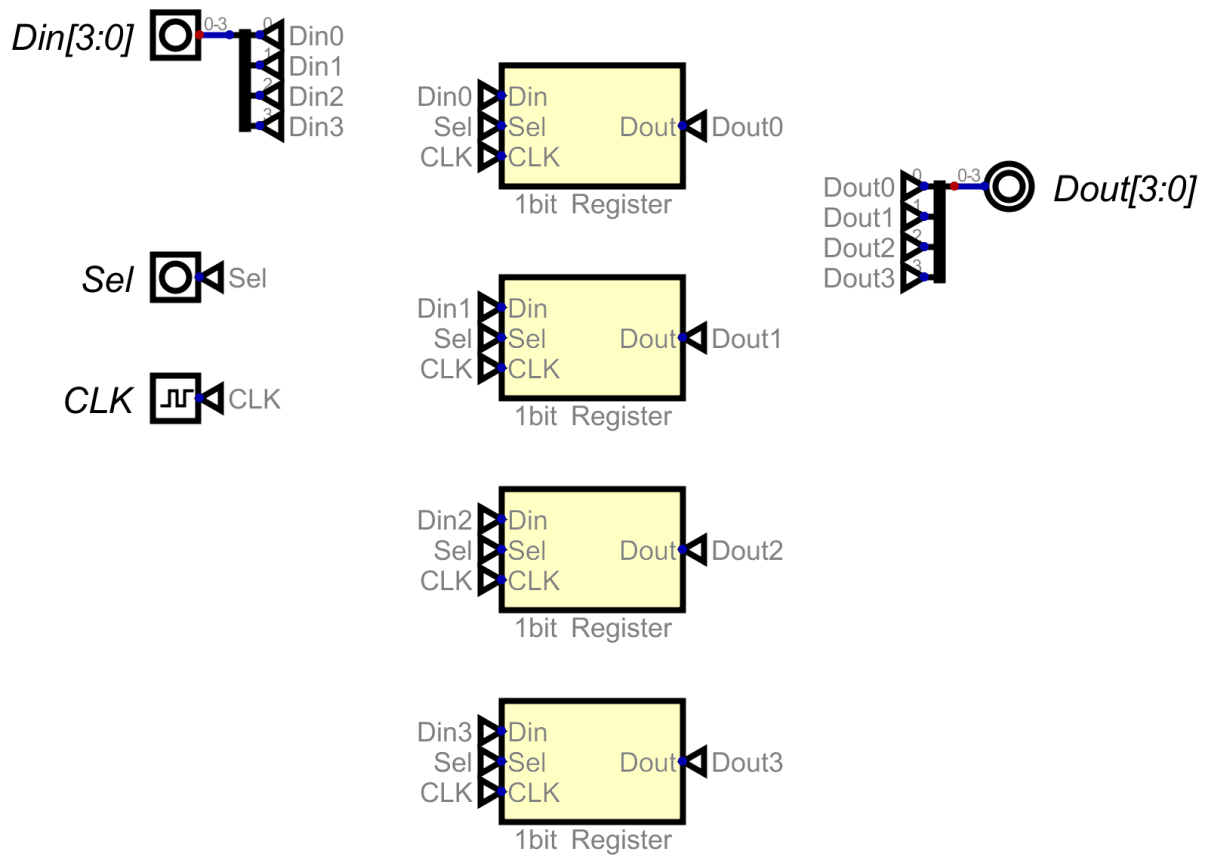


Figure: 4bit Register

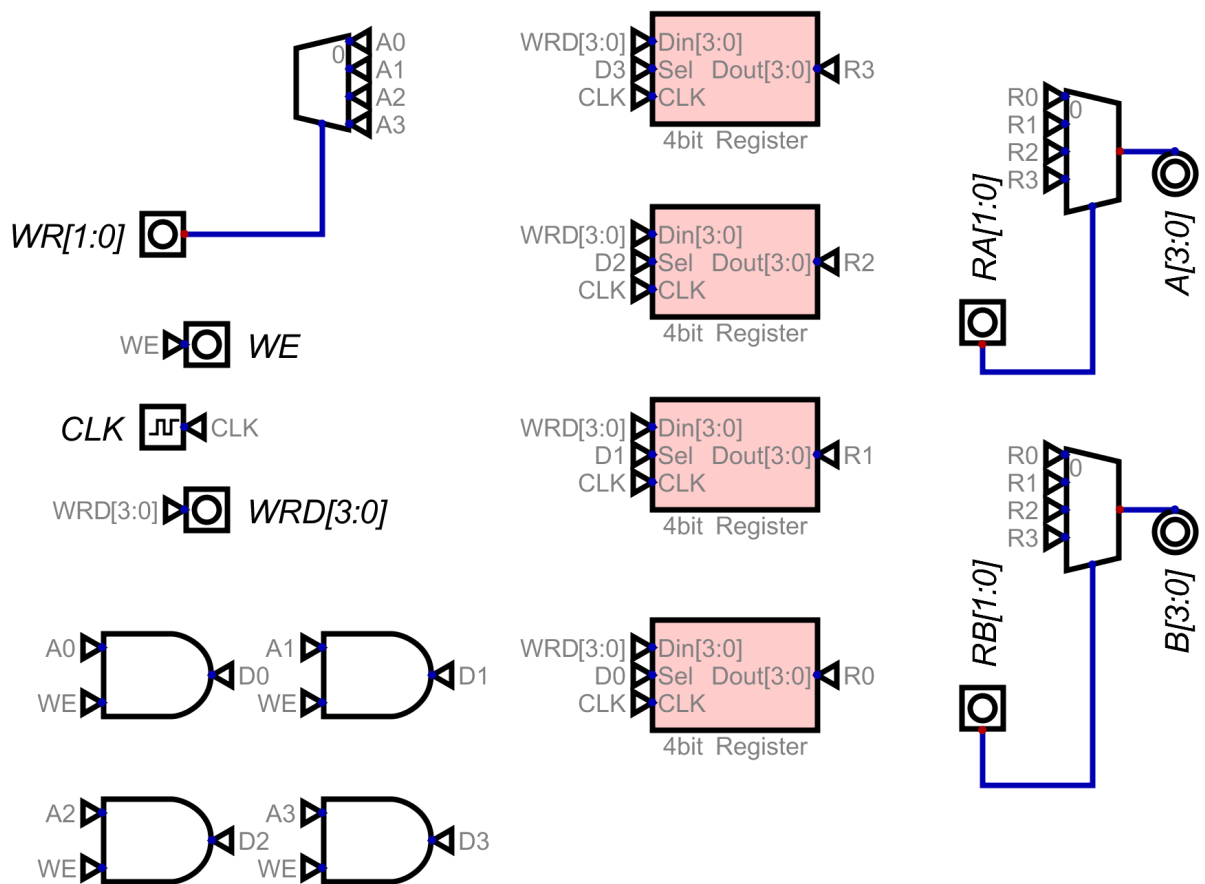


Figure: 4bit register_set

3. RAM Circuit (Top to Bottom all circuits):

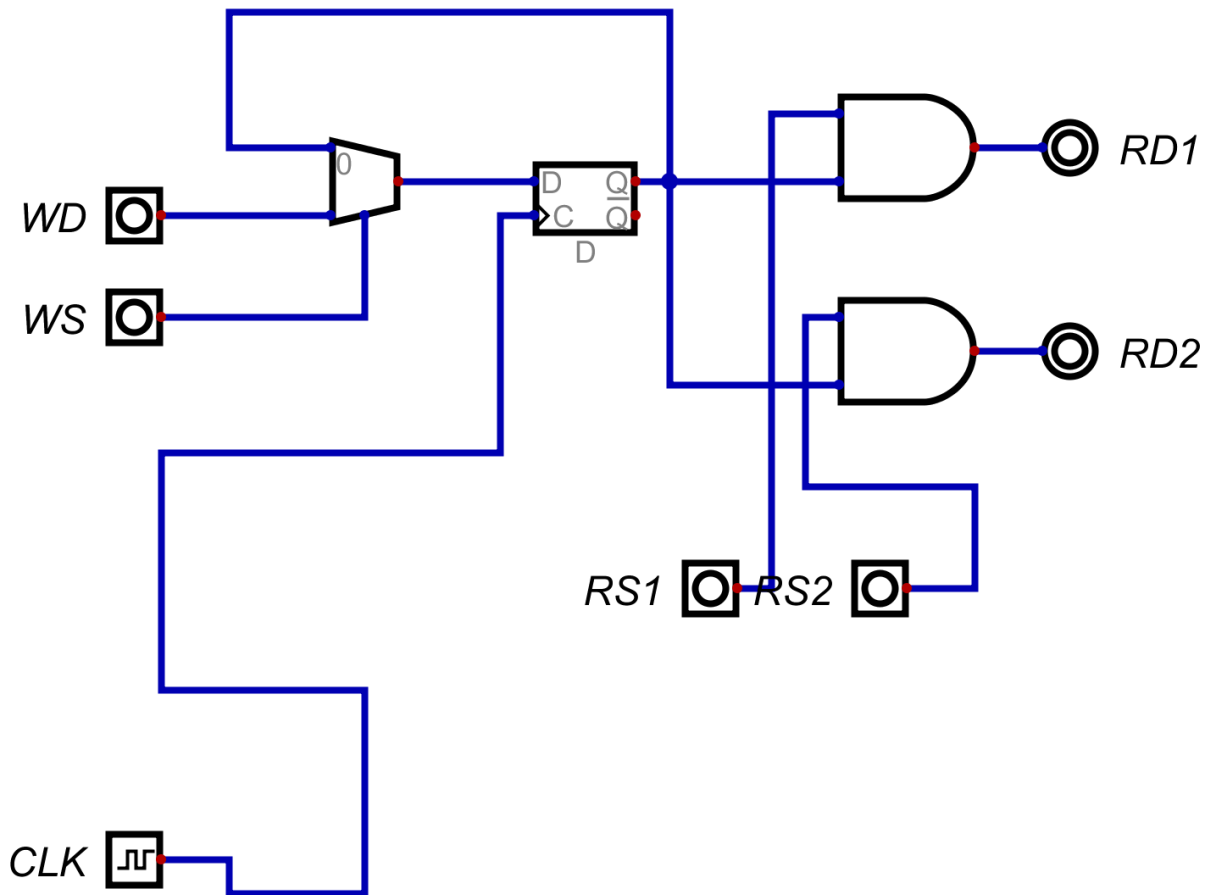


Figure: 1X1 SRAM

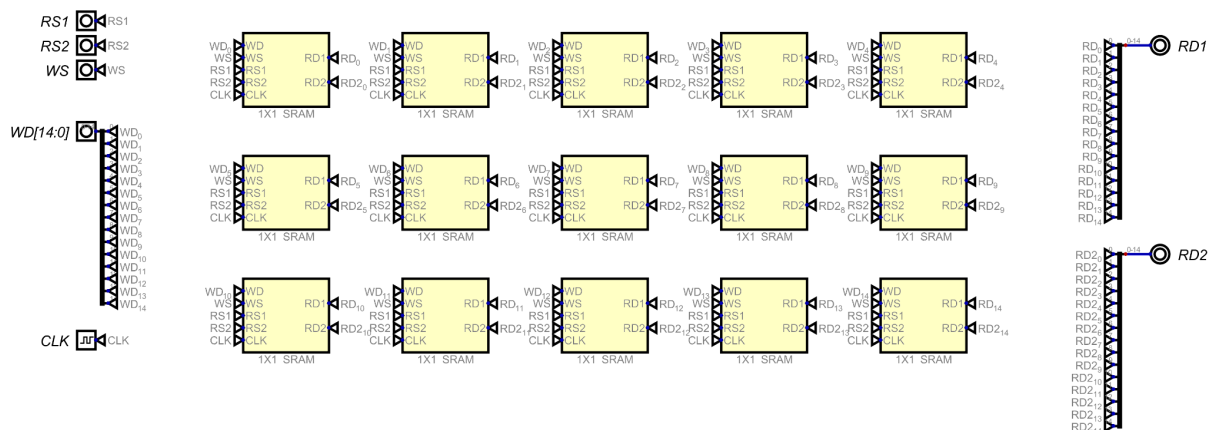


Figure: 1X15 SRAM

 


Figure: 7X15 SRAM

4. ISA:

Opcode (4 bit)		Register 1	Register 2	Assembly Example
Type (2 bits)	Operations (2 bits)	2 bits	2 bits	
00	00 (ROR)	00-11(R0-R3)	00-11(R0-R3)	ROR R0, R1
	01 (XOR)	00-11(R0-R3)	00-11(R0-R3)	XOR R2, R3
	10 (ADD)	00-11(R0-R3)	00-11(R0-R3)	ADD R0, R1

ISA(Register Mode)

Opcode (4 bit)		Register 1	Constant	Assembly Example
Type (2 bits)	Operations (2 bits)	2 bits	4 bits	
01	00 (ROR)	00-11(R0-R3)	0000-1111 (0-15)	ROR R0, 1
	01 (XOR)	00-11(R0-R3)	0000-1111 (0-15)	XOR R2, 2
	10 (ADD)	00-11(R0-R3)	0000-1111 (0-15)	ADD R0, 3

ISA(Immediate Mode)

Opcode (4 bit)		Address	Register 1	Assembly Example
Type (2 bits)	Operations (2 bits)	3 bits	2 bits	
10	00 (JMP)	00-11(R0-R3)	00-11(0-3)	JMP LABEL
	01(JG)	00-11(R0-R3)	00-11(0-3)	JG LABEL

ISA(Branching)

5. CPU (Top to Bottom all circuits):

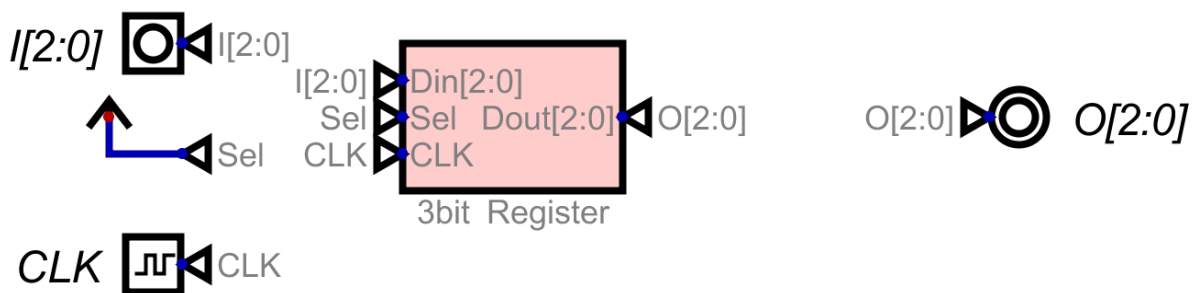


Figure: Program Counter

 


Figure: AddOne Circuit

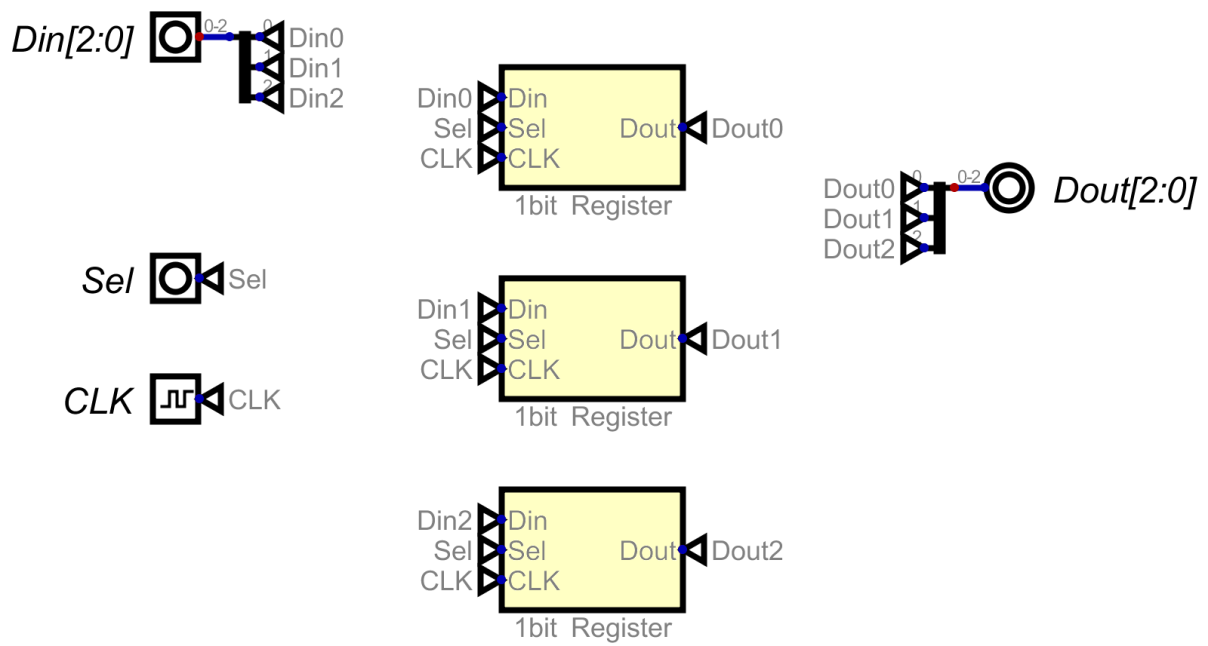


Figure: 3bit Register

 


Figure: 7X15 SRAM

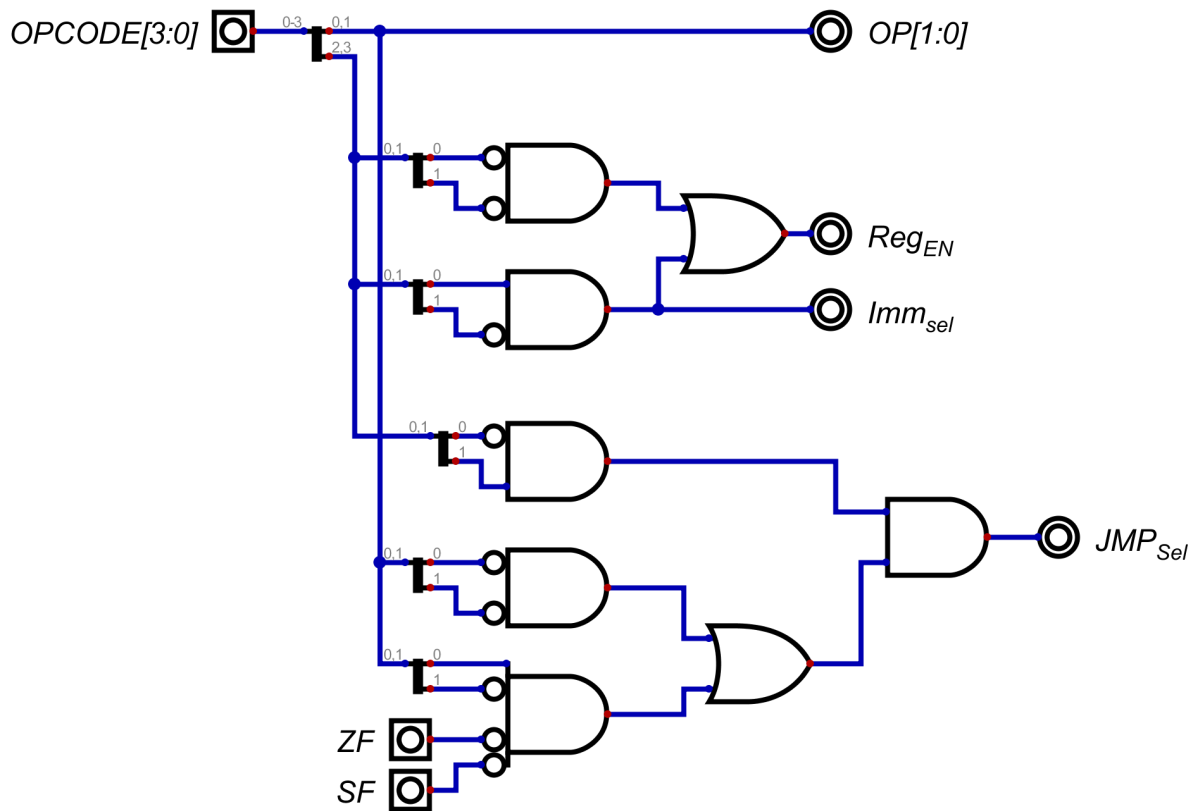


Figure: Control unit

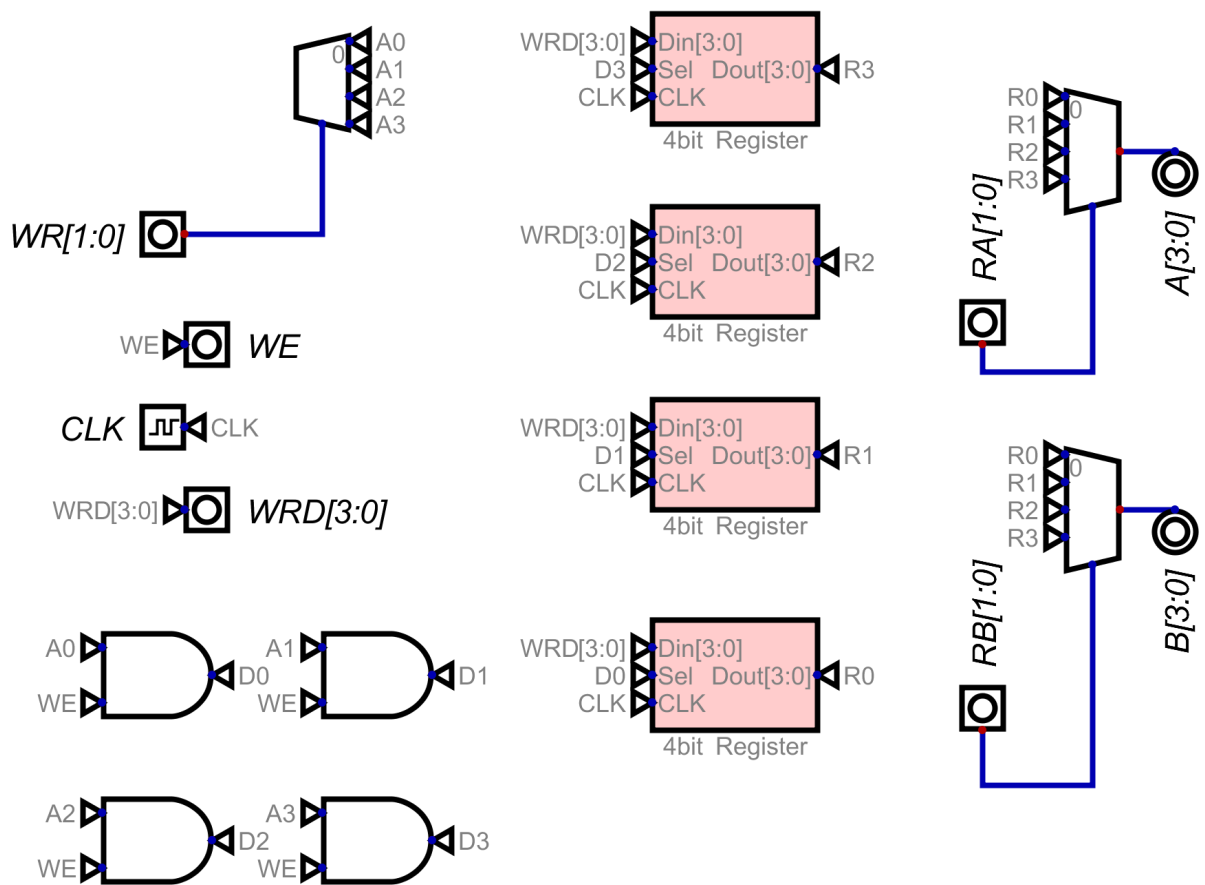


Figure: 4bit register_set

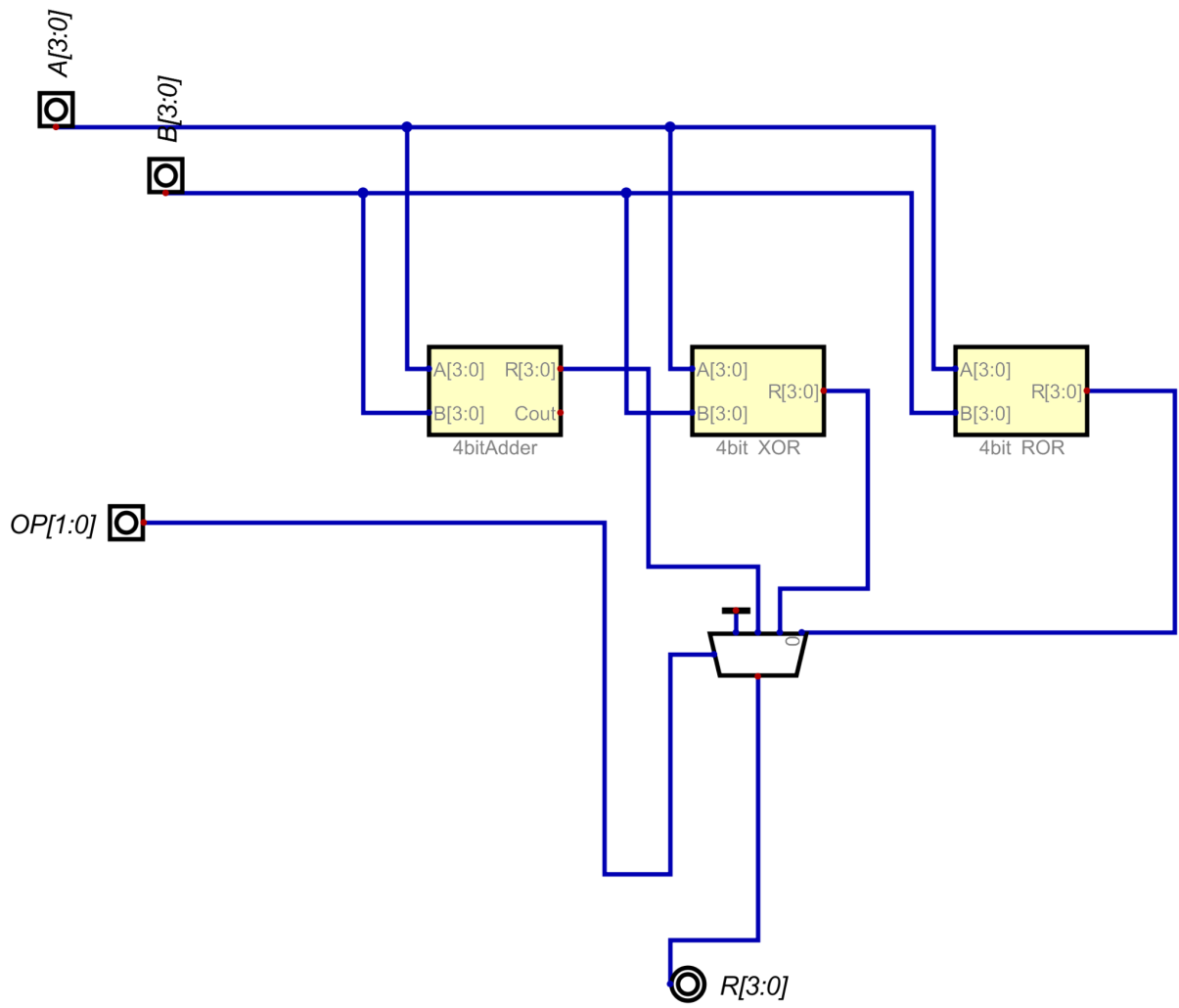


Figure: ALU

Verilog Code:

1. **ALU Circuit (Top to Bottom all circuits):**

2. **Register Set Circuit (Top to Bottom all circuits):**

3. **RAM Circuit (Top to Bottom all circuits):**

4. **CPU (Top to Bottom all circuits):**